



# COE 272


# Digital Systems

Lecture 4: Logic Implementation using resistors, Diodes and Transistors



# EXAMPLE OF CIRCUIT WITH AND ,OR and NOT GATES


$$F(a,b,c,d) = ab + cd' + ab'c'd$$



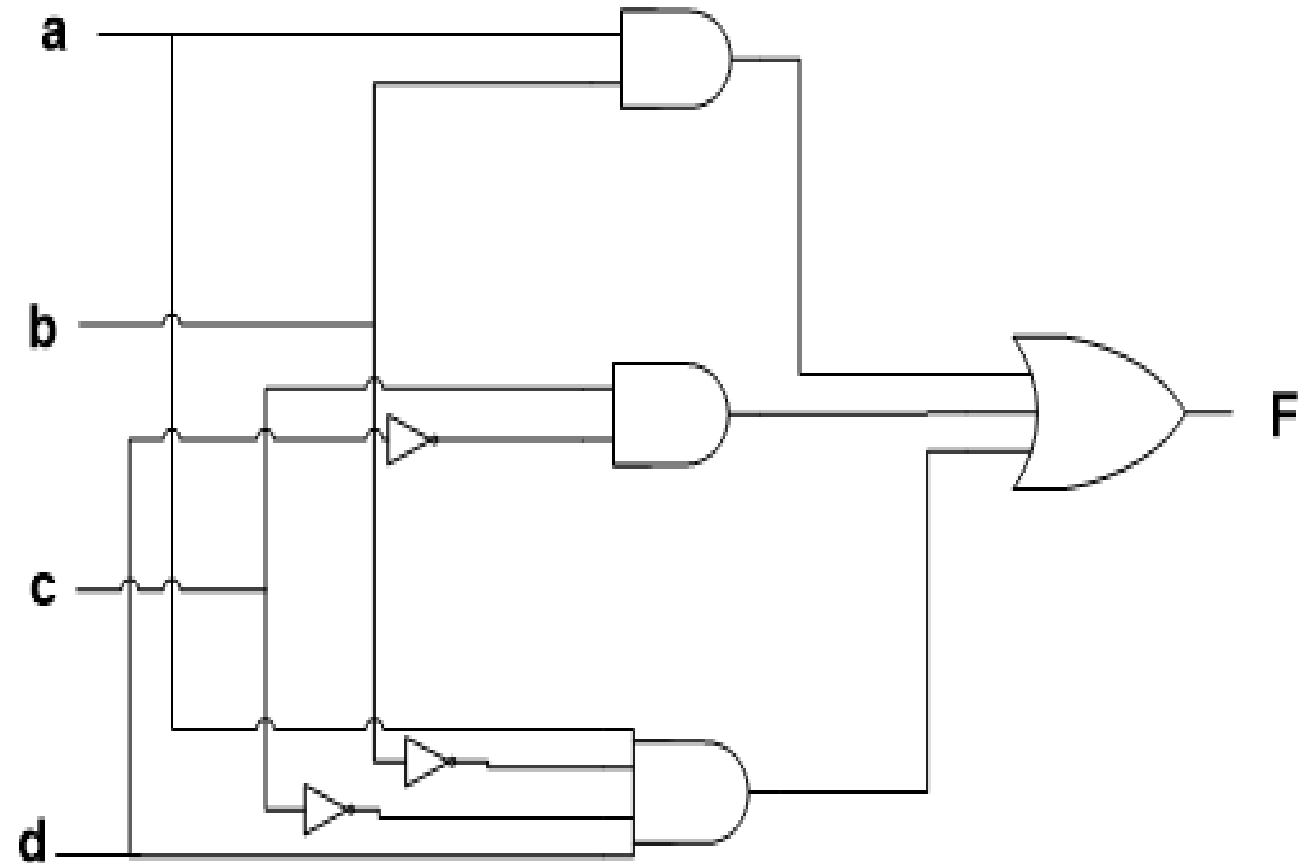




# OTHER DERIVED GATES

- NAND (NOT AND)

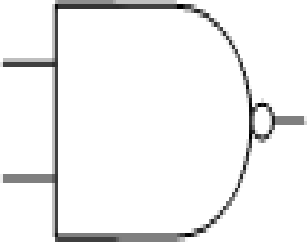
Operation	Gate Symbol	Algebraic Equation	Truth Table															
NAND		$F = \overline{XY}$	<table border="1"><thead><tr><th>X</th><th>Y</th><th>F</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	X	Y	F	0	0	1	0	1	1	1	0	1	1	1	0
X	Y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																

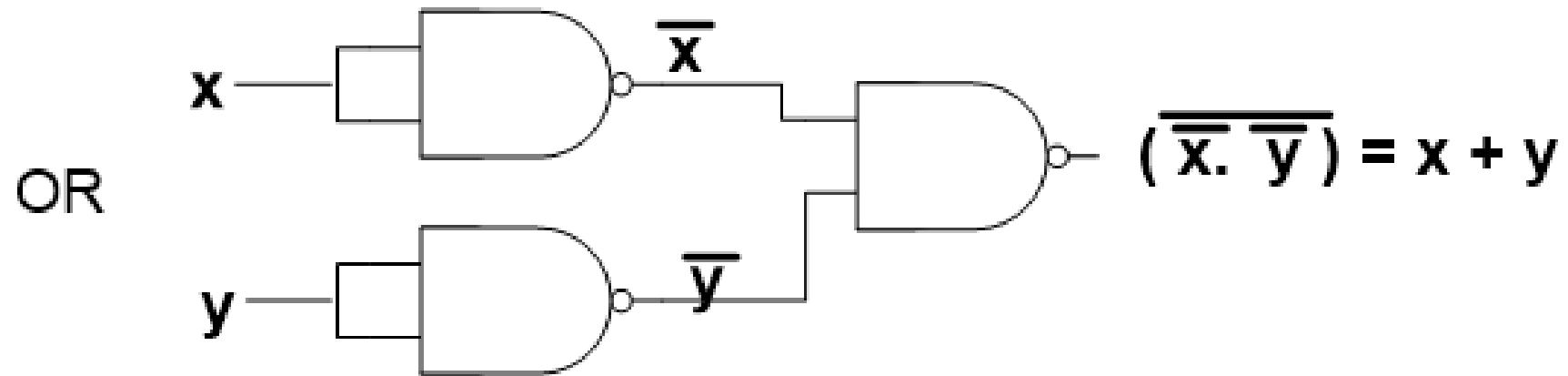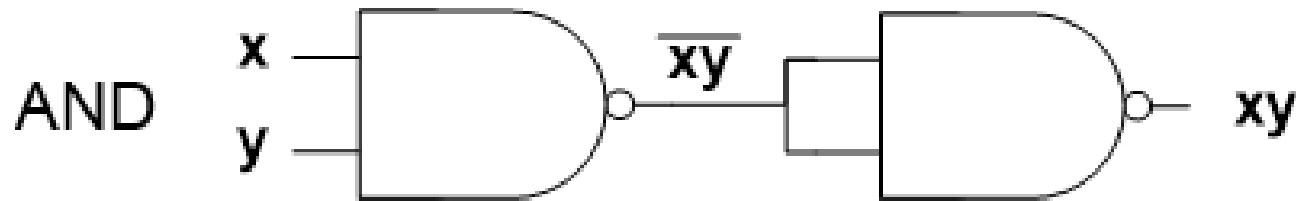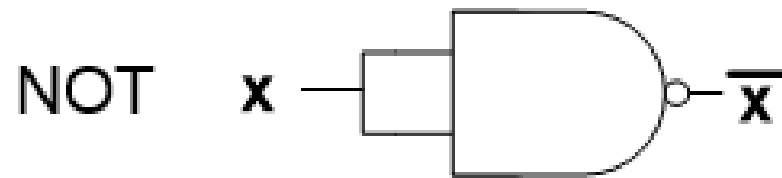



# NOR OPERATION (NOT OR)

NOR

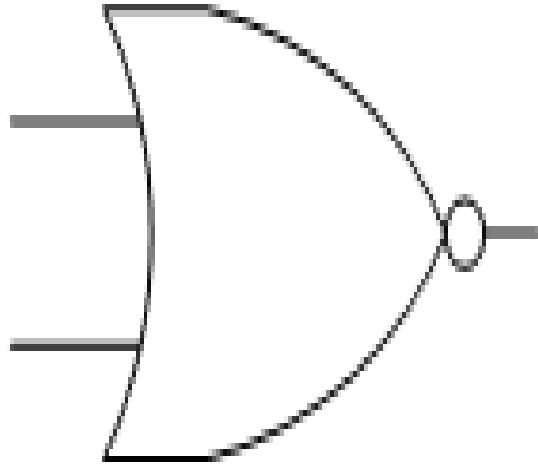


$$F = \overline{X+Y}$$


X	Y	F
0	0	1
0	1	0
1	0	0
1	1	0




NOT

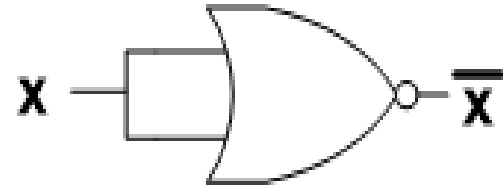

AND

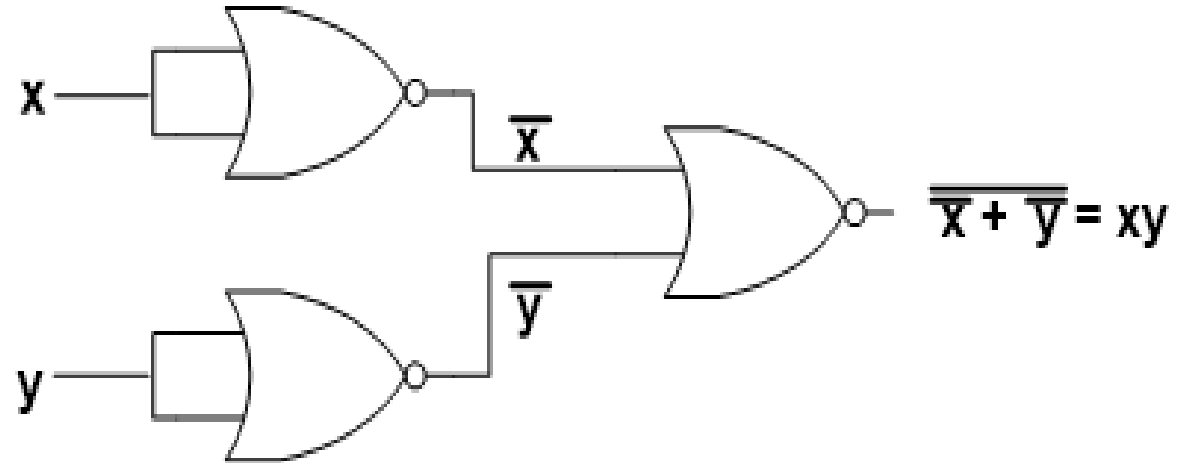

OR

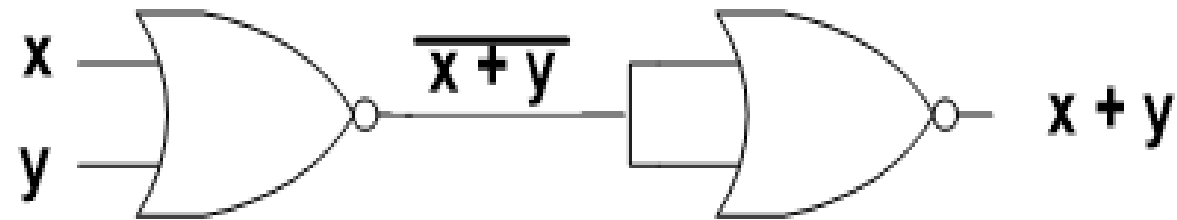




# EXCLUSIVE OR (XOR) OPERATION

Operation      Gate Symbol      Algebraic Equation      Truth Table

XOR

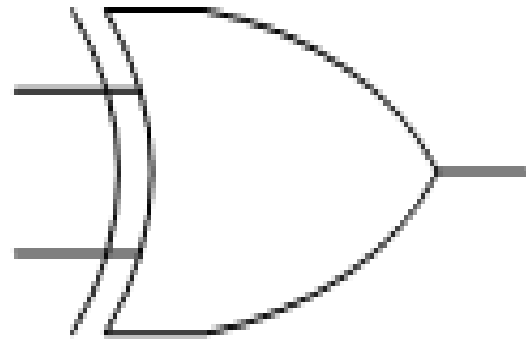

$$F = X \oplus Y$$

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	0

$$x \oplus y = x\bar{y} + \bar{x}y$$



# XOR OPERATION

$$x \oplus 0 = x$$

$$x \oplus x = 0$$

$$x \oplus \overline{y} = \overline{x \oplus y}$$

$$x \oplus 1 = \overline{x}$$

$$x \oplus \overline{x} = 1$$


$$\overline{x} \oplus y = \overline{x \oplus y}$$





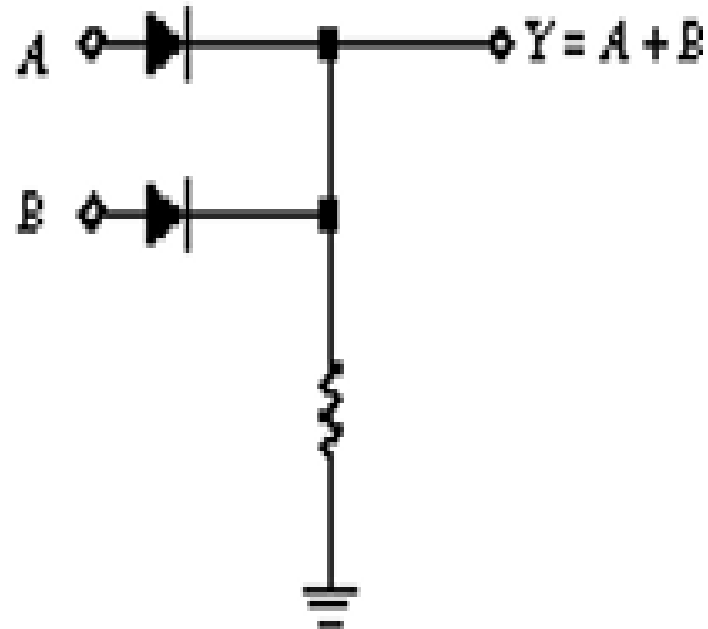
# DIODE LOGIC

- We can construct simple gates with the use of diodes and resistors.
- Below is an OR gate constructed with the use of diodes and resistors.






# AND gate

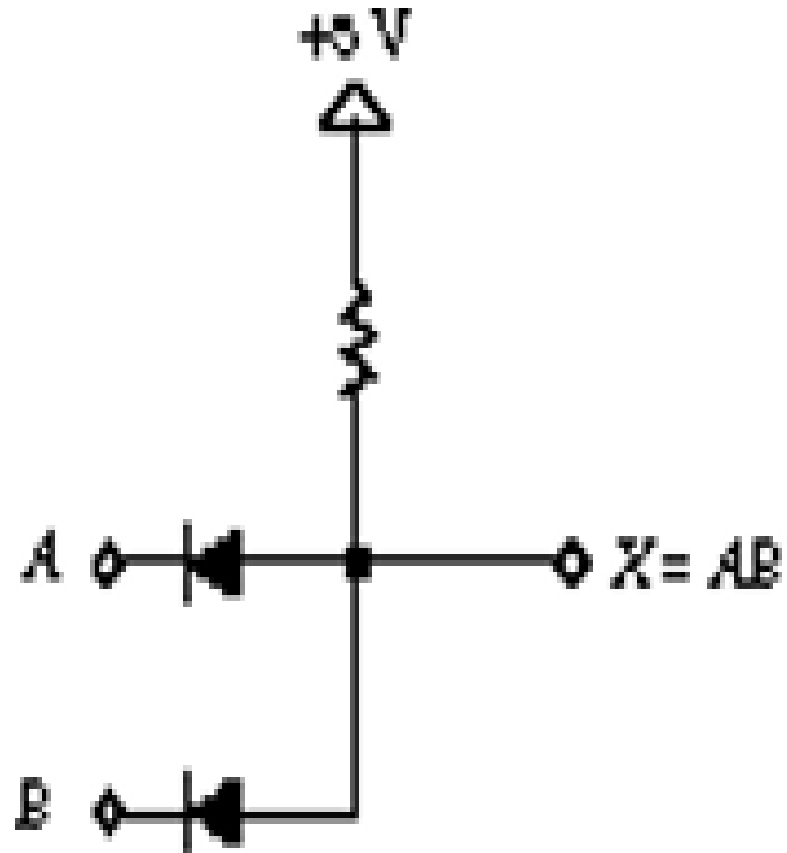



# BIPOLAR TRANSISTOR LOGIC (BJT)


- BASIC INVERTER

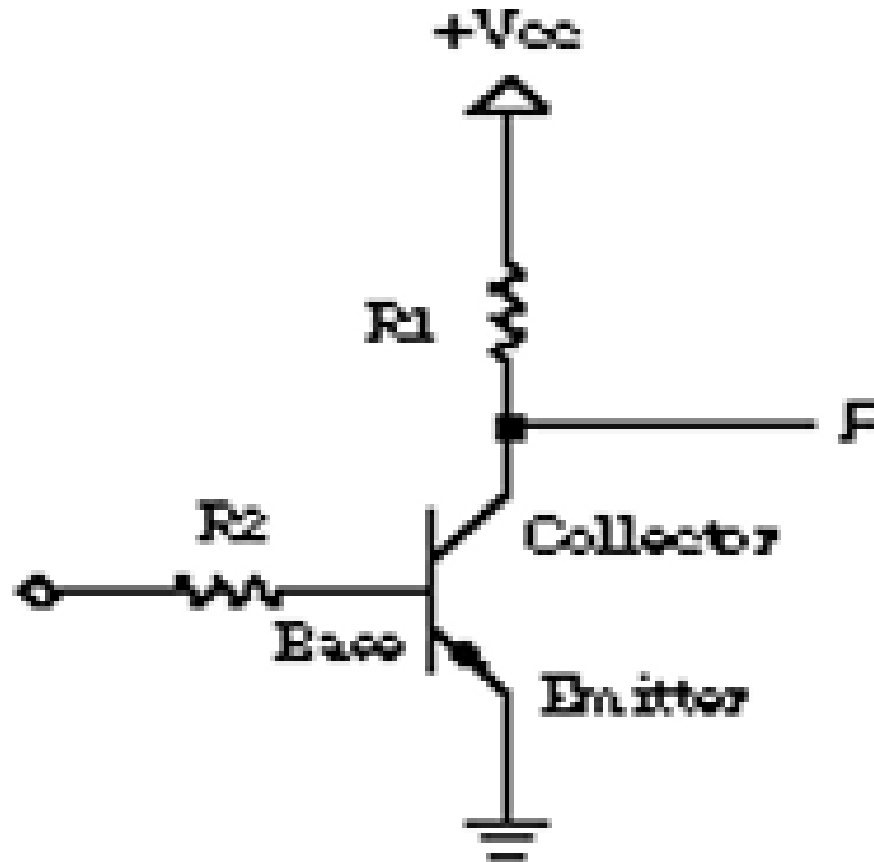



# DIODE TRANSISTOR LOGIC (DTL)


- A 2 input DTL NAND gate

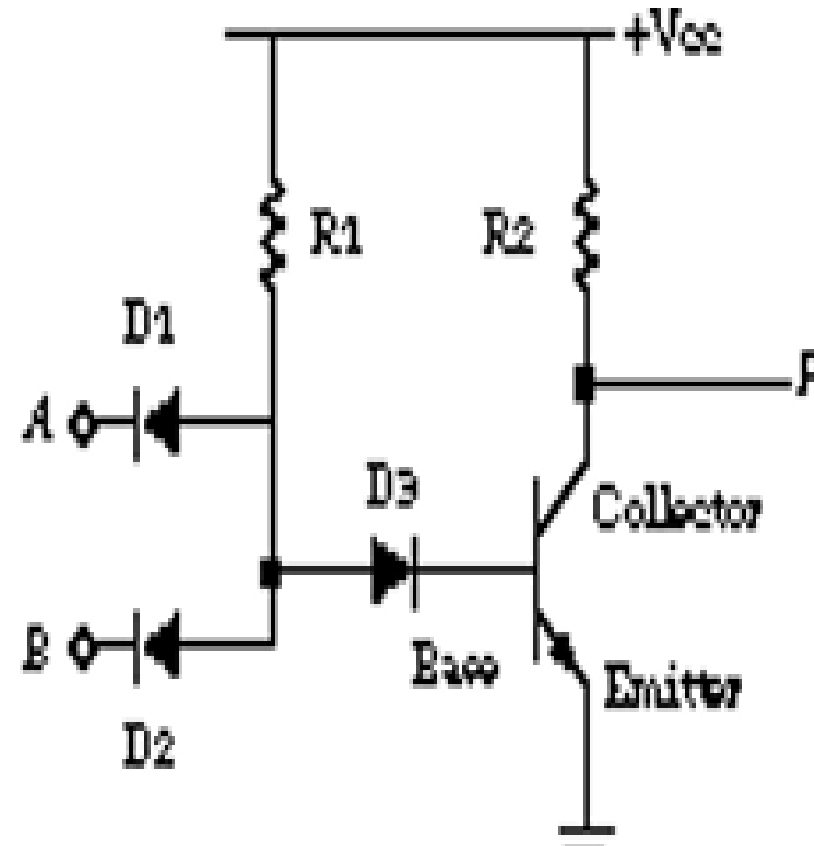




# TRANSISTOR – TRANSISTOR LOGIC (TTL)

- A 2 INPUT TTL NAND GATE

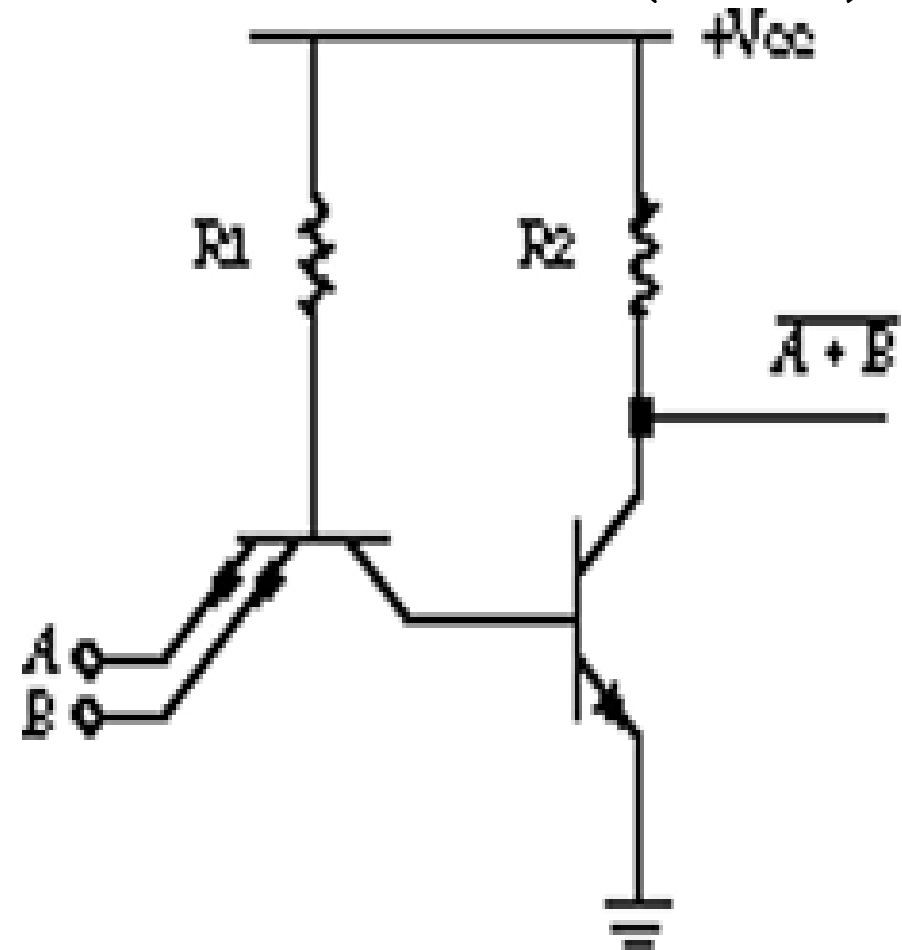





# LOGIC GATES FROM MOS DEVICES

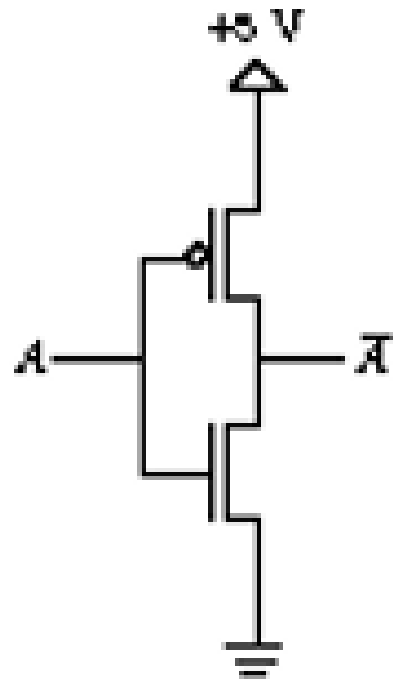

(a) Inverter

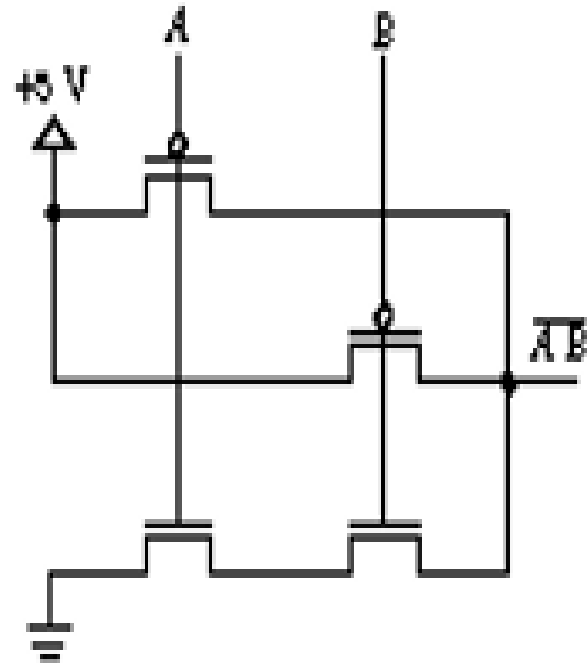

(b) NAND

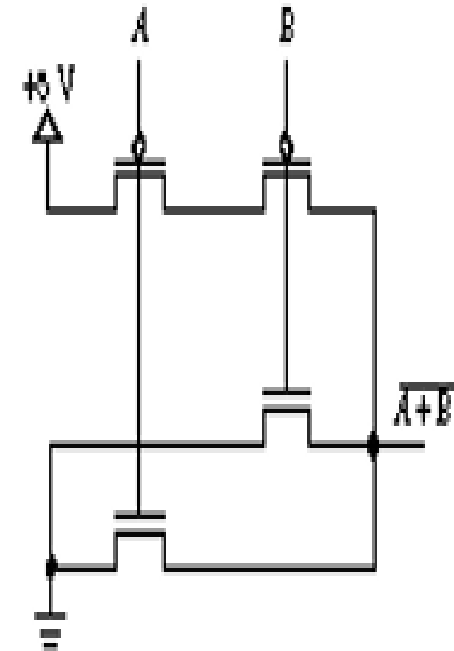

(c) NOR



# THE BUFFER GATE

- This is helpful in boosting weak signals to enable them drive a resistance load if required.

*Double inversion*

