



# COE 272

# Digital Systems

Sequential Circuits

(Memory Elements – Latches & Flip Flops)




# Overview

- Introduction
- Memory Elements
- Pulse-Triggered Latch
  - S-R Latch
  - Gated S-R Latch
  - Gated D Latch
- Edge-Triggered Flip-flops
  - S-R Flip-flop
  - D Flip-flop
  - J-K Flip-flop
  - T Flip-flop
- Asynchronous Inputs


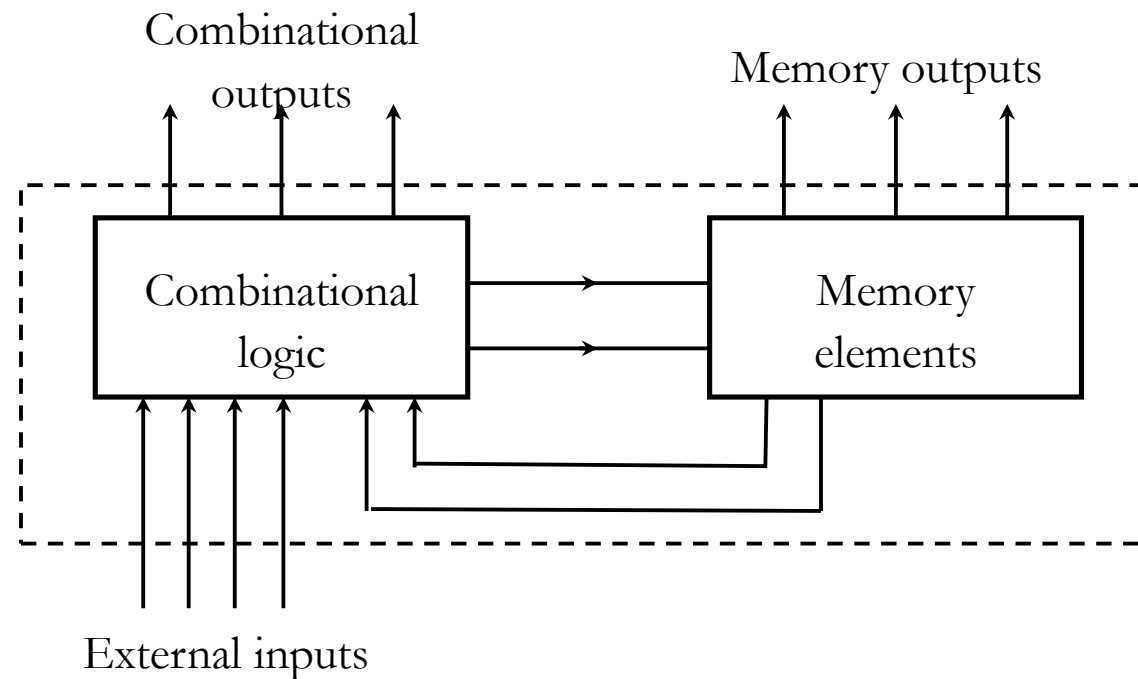
# Introduction

- A **sequential circuit** consists of a *feedback path*, and employs some *memory elements*.



Sequential circuit = Combinational logic + Memory Elements




# Introduction

- There are two types of sequential circuits:
  - *synchronous*: outputs change only at specific time
  - *asynchronous*: outputs change at any time
- *Multivibrator*: a class of sequential circuits. They can be:
  - *bistable* (2 stable states)
  - *monostable* or *one-shot* (1 stable state)
  - *astable* (no stable state)
- Bistable logic devices: *latches* and *flip-flops*.
- Latches and flip-flops differ in the method used for changing their state.


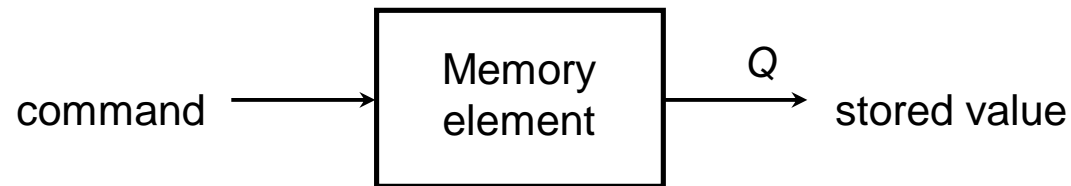
# Memory Elements

- **Memory element:** a device which can remember value indefinitely, or change value on command from its inputs.



- **Characteristic table:**


Command (at time $t$ )	$Q(t)$	$Q(t+1)$
Set	X	1
Reset	X	0
Memorise / No Change	0	0
	1	1

$Q(t)$ : current state  
 $Q(t+1)$  or  $Q^+$ : next state



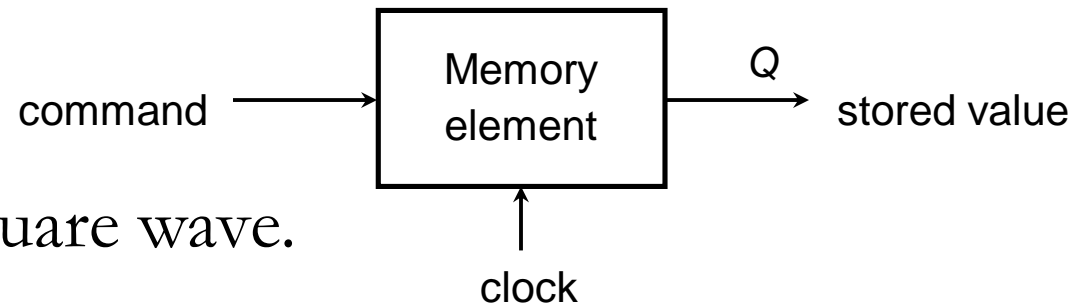
# Memory Elements

- Memory element with clock. Flip-flops are memory elements that change state on clock signals.



- Clock is usually a square wave.

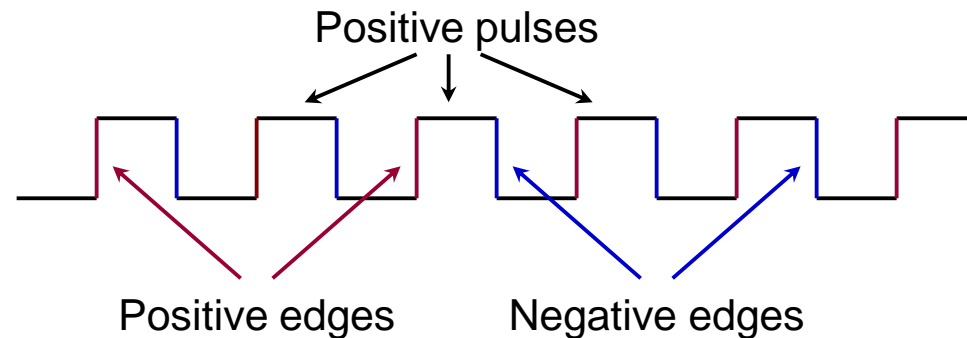



# Memory Elements

- Two types of triggering/activation:
  - pulse-triggered
  - edge-triggered
- Pulse-triggered
  - latches
  - ON = 1, OFF = 0
- Edge-triggered
  - flip-flops
  - positive edge-triggered (ON = from 0 to 1; OFF = other time)
  - negative edge-triggered (ON = from 1 to 0; OFF = other time)



# S-R Latch

- *Complementary* outputs:  $Q$  and  $Q'$ .
- When  $Q$  is HIGH, the latch is in *SET* state.
- When  $Q$  is LOW, the latch is in *RESET* state.
- For *active-HIGH input S-R latch* (also known as NOR gate latch),
  - $R=HIGH$  (and  $S=LOW$ )  $\Rightarrow$  RESET state
  - $S=HIGH$  (and  $R=LOW$ )  $\Rightarrow$  SET state
  - both inputs LOW  $\Rightarrow$  no change
  - both inputs HIGH  $\Rightarrow$   $Q$  and  $Q'$  both LOW (invalid)!





# S-R Latch


- For *active-LOW input S'-R' latch* (also known as NAND gate latch),
  - $R'=LOW$  (and  $S'=HIGH$ )  $\Leftrightarrow$  RESET state
  - $S'=LOW$  (and  $R'=HIGH$ )  $\Leftrightarrow$  SET state
  - both inputs HIGH  $\Leftrightarrow$  no change
  - both inputs LOW  $\Leftrightarrow Q$  and  $Q'$  both HIGH (invalid)!
- Drawback of S-R latch: invalid condition exists and must be avoided.



# S-R Latch


- Characteristics table for active-high input S-R latch:

S	R	Q	Q'	
0	0	NC	NC	No change. Latch remained in present state.
1	0	1	0	Latch SET.
0	1	0	1	Latch RESET.
1	1	0	0	Invalid condition.

 

- Characteristics table for active-low input S'-R' latch:


S'	R'	Q	Q'	
1	1	NC	NC	No change. Latch remained in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition.

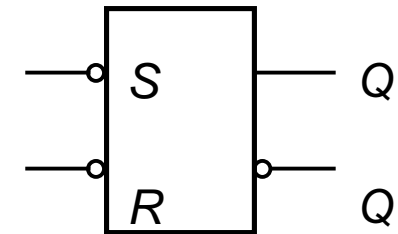




# S-R Latch

- Active-HIGH input S-R latch

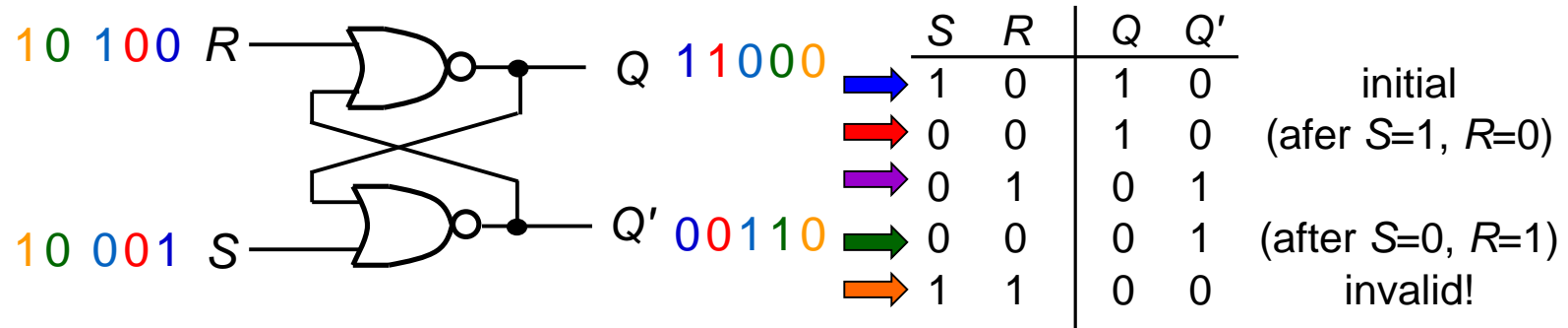



- Active-LOW input S'-R' latch

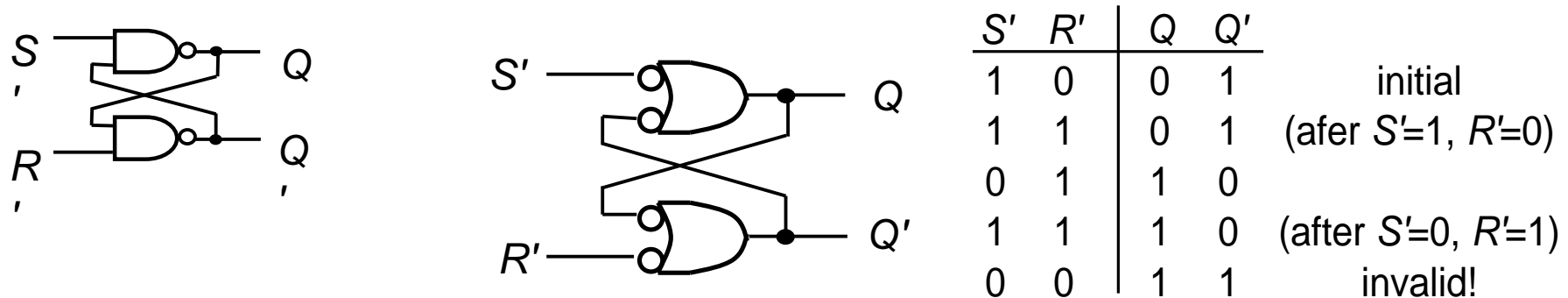


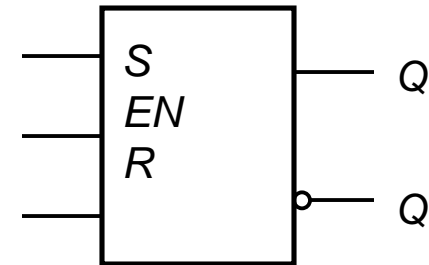 
# Gated S-R Latch

- S-R latch + *enable input (EN)* and 2 NAND gates → *gated S-R latch*.





# Gated S-R Latch

- Outputs change (if necessary) only when  $EN$  is HIGH.
- Under what condition does the invalid state occur?
- Characteristic table:

$EN=1$

$Q(t)$	$S$	$R$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate

$S$	$R$	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	indeterminate	



$$Q(t+1) = S + R'.Q$$

$$S.R = 0$$


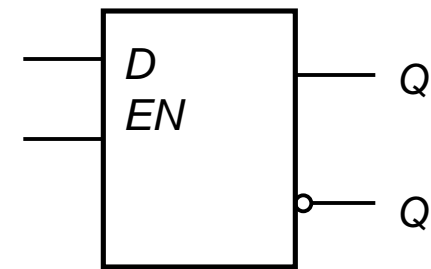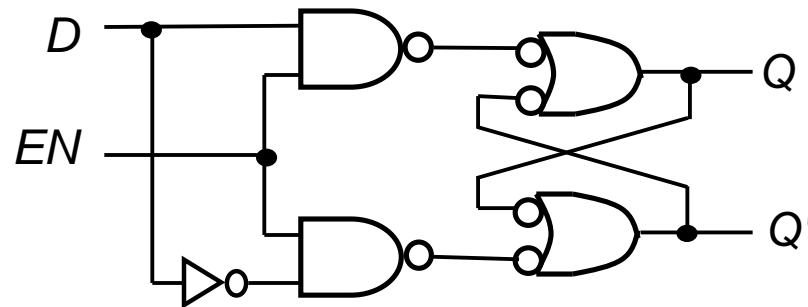
# Gated D Latch

- Make  $R$  input equal to  $S'$   $\rightarrow$  *gated D latch*.
- $D$  latch eliminates the undesirable condition of invalid state in the  $S$ - $R$  latch.





# Gated D Latch

- When  $EN$  is HIGH,
  - $D=HIGH \rightarrow$  latch is SET
  - $D=LOW \rightarrow$  latch is RESET
- Hence when  $EN$  is HIGH,  $Q$  'follows' the  $D$  (data) input.
- Characteristic table:

$EN$	$D$	$Q(t+1)$	
1	0	0	Reset
1	1	1	Set
0	X	$Q(t)$	No change

When  $EN=1$ ,  $Q(t+1) = D$



# Latch Circuits: Not Suitable


- Latch circuits are not suitable in synchronous logic circuits.
- When the enable signal is active, the excitation inputs are gated directly to the output Q. Thus, any change in the excitation input immediately causes a change in the latch output.
- The problem is solved by using a special timing control signal called a *clock* to restrict the times at which the states of the memory elements may change.
- This leads us to the edge-triggered memory elements called *flip-flops*.




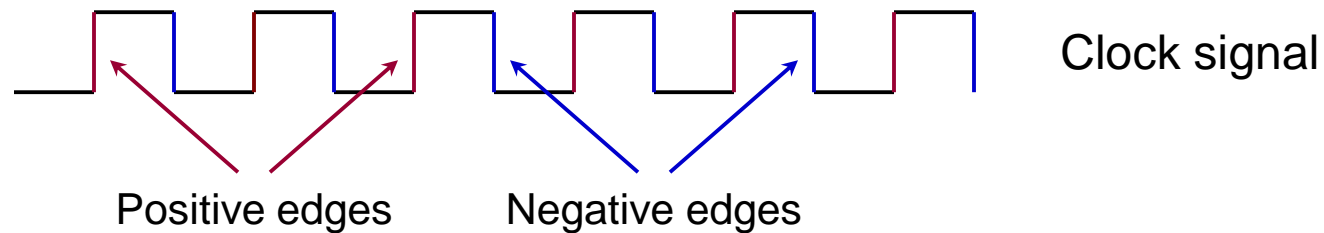
# Edge-Triggered Flip-flops


- *Flip-flops*: synchronous bistable devices
- Output changes state at a specified point on a triggering input called the *clock*.
- Change state either at the *positive edge* (rising edge) or at the *negative edge* (*falling edge*) of the clock signal.





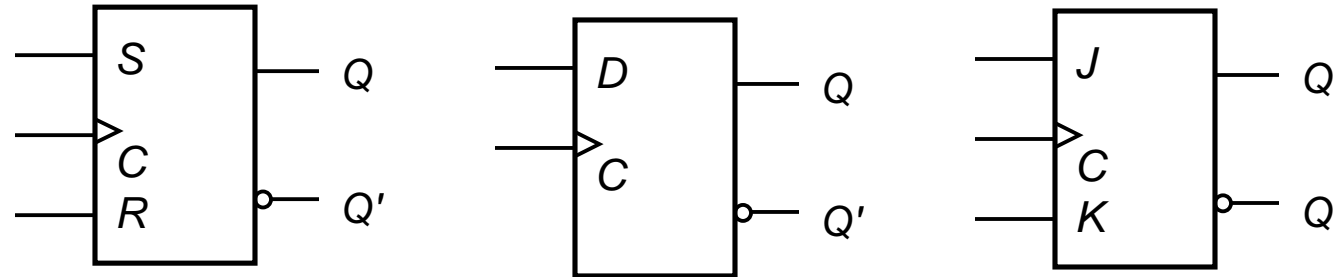
# Edge-Triggered Flip-flops

- S-R, D and J-K edge-triggered flip-flops. Note the “>” symbol at the clock input.



Positive edge-triggered flip-flops

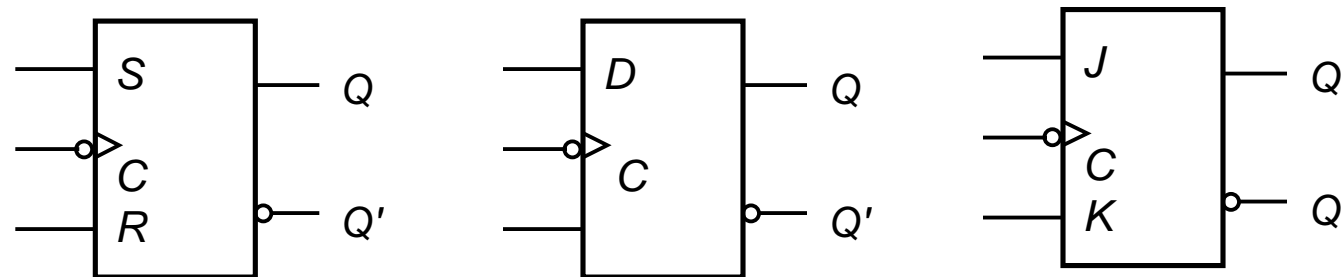

Negative edge-triggered flip-flops



# S-R Flip-flop

- **S-R flip-flop**: on the triggering edge of the clock pulse,
  - $S=HIGH$  (and  $R=LOW$ ) a SET state
  - $R=HIGH$  (and  $S=LOW$ ) a RESET state
  - both inputs LOW a no change
  - both inputs HIGH a invalid
- Characteristic table of positive edge-triggered S-R flip-flop:

<b>S</b>	<b>R</b>	<b>CLK</b>	<b>Q(t+1)</b>	<b>Comments</b>
0	0	X	Q(t)	No change
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	?	Invalid

X = irrelevant (“don’t care”)

↑ = clock transition LOW to HIGH






# S-R Flip-flop

- It comprises 3 parts:
  - a basic *NAND latch*
  - a *pulse-steering* circuit
  - a *pulse transition detector* (or *edge detector*) circuit
- The **pulse transition detector** detects a rising (or falling) edge and produces a very *short-duration spike*.





# S-R Flip-flop

The pulse transition detector.

  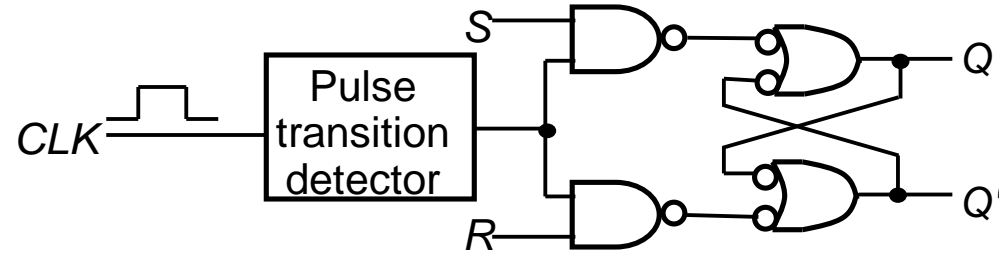

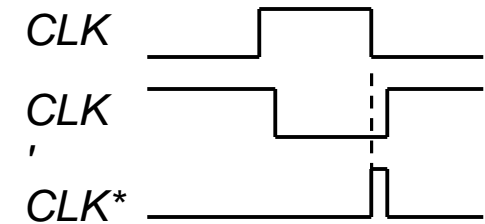 Positive-going transition  
(rising edge)




Negative-going transition  
(falling edge)


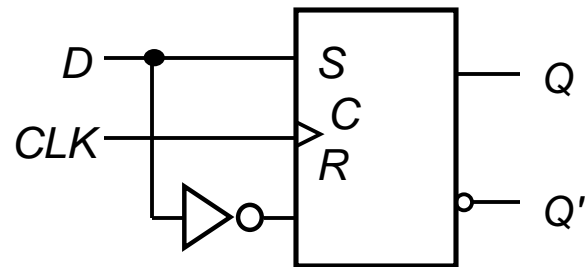
# D Flip-flop

- **D flip-flop**: single input  $D$  (data)
  - $D=HIGH \Rightarrow$  SET state
  - $D=LOW \Rightarrow$  RESET state
- $Q$  follows  $D$  at the clock edge.
- Convert S-R flip-flop into a D flip-flop: add an inverter.



A positive edge-triggered D flip-flop formed with an S-R flip-flop.

$D$	$CLK$	$Q(t+1)$	Comments
1	↑	1	Set
0	↑	0	Reset


↑ = clock transition LOW to HIGH


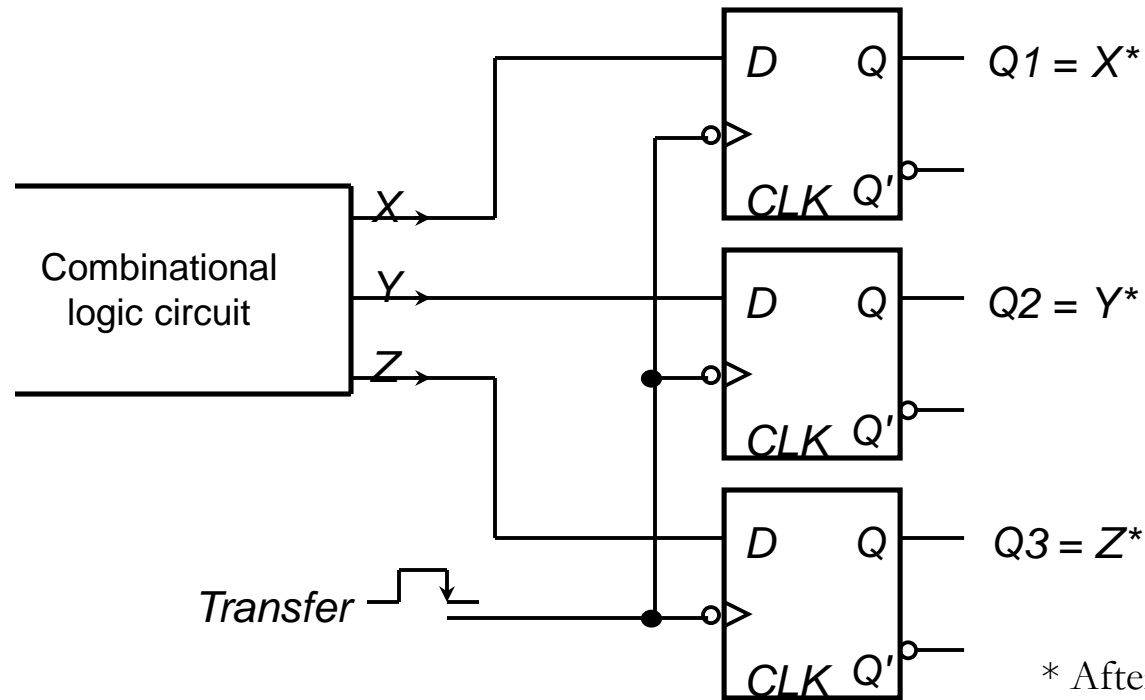
# D Flip-flop

- Application: *Parallel data transfer.*

To transfer logic-circuit outputs  $X$ ,  $Y$ ,  $Z$  to flip-flops  $Q_1$ ,  $Q_2$  and  $Q_3$  for storage.



\* After occurrence of negative-going transition



# J-K Flip-flop


- **J-K flip-flop**: Q and Q' are fed back to the pulse-steering NAND gates.
- No invalid state.
- Include a *toggle* state.
  - $J=\text{HIGH}$  (and  $K=\text{LOW}$ )  $\Leftrightarrow$  SET state
  - $K=\text{HIGH}$  (and  $J=\text{LOW}$ )  $\Leftrightarrow$  RESET state
  - both inputs LOW  $\Leftrightarrow$  no change
  - both inputs HIGH  $\Leftrightarrow$  toggle





# J-K Flip-flop

- J-K flip-flop.

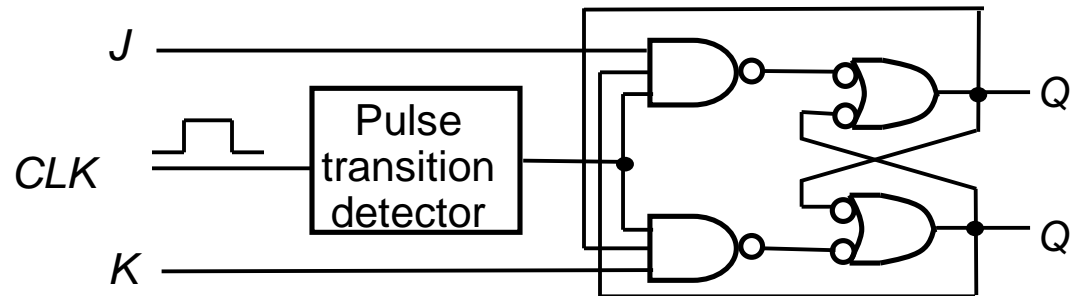

- Characteristic table.

J	K	CLK	Q(t+1)	Comments
0	0	↑	Q(t)	No change
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	Q(t)'	Toggle



$$Q(t+1) = J \cdot Q' + K' \cdot Q$$

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


  
# T Flip-flop

- **T flip-flop**: single-input version of the J-K flip flop, formed by tying both inputs together.



- Characteristic table.

$T$	$CLK$	$Q(t+1)$	Comments
0	↑	$Q(t)$	No change
1	↑	$Q(t)'$	Toggle


$$Q(t+1) = T \cdot Q' + T' \cdot Q$$

$Q$	$T$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0




# T Flip-flop

- Application: *Frequency division.*

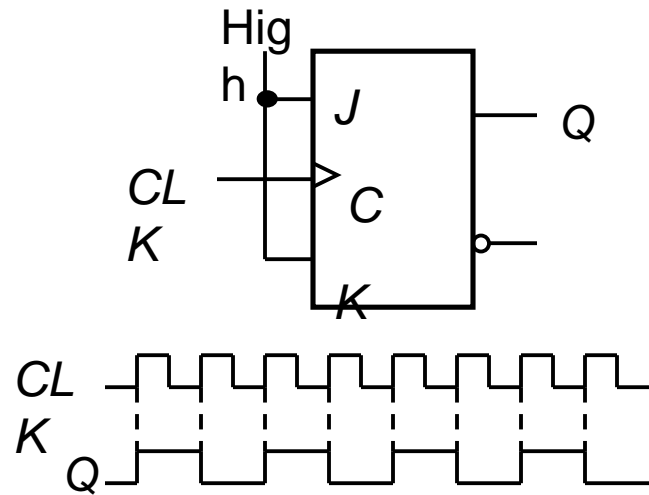

Divide clock frequency by 2.

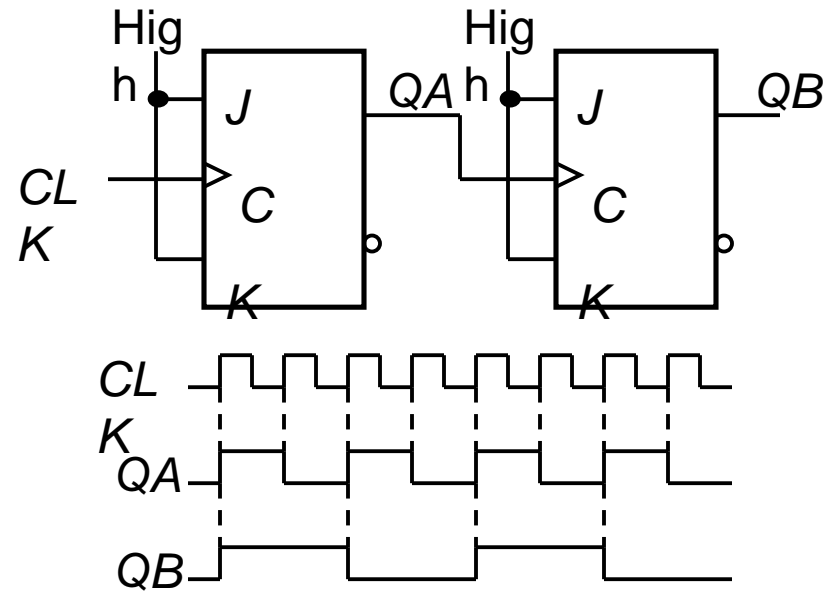

Divide clock frequency by 4.

- Application: *Counter* (to be covered in next lecture.)



# Asynchronous Inputs

- S-R, D and J-K inputs are synchronous inputs, as data on these inputs are transferred to the flip-flop's output only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock; example: *preset (PRE)* and *clear (CLR)* [or *direct set (SD)* and *direct reset (RD)*]
- When  $PRE=HIGH$ ,  $Q$  is immediately set to HIGH.
- When  $CLR=HIGH$ ,  $Q$  is immediately cleared to LOW.
- Flip-flop in normal operation mode when both  $PRE$  and  $CLR$  are LOW.



# Asynchronous Inputs

- A J-K flip-flop with active-LOW preset and clear inputs.

